
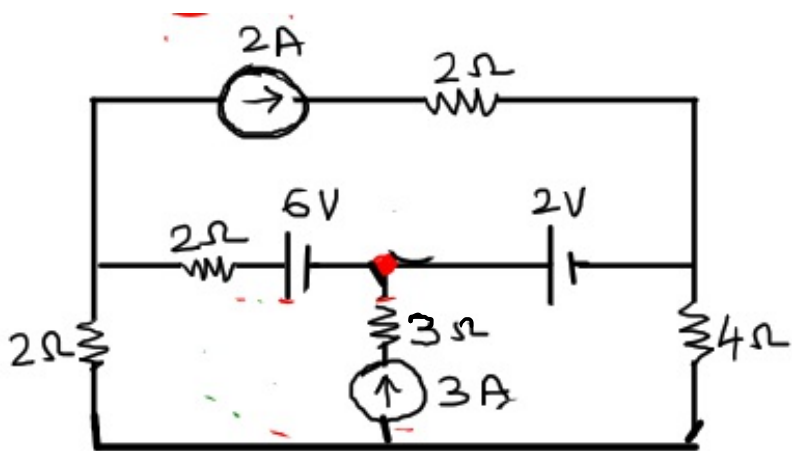


1. Find Current Flowing in 4 Ohm Resistor using Mesh/Nodal/ Thevenin's/ Norton's /Superposition Method/ source transformation.

1A

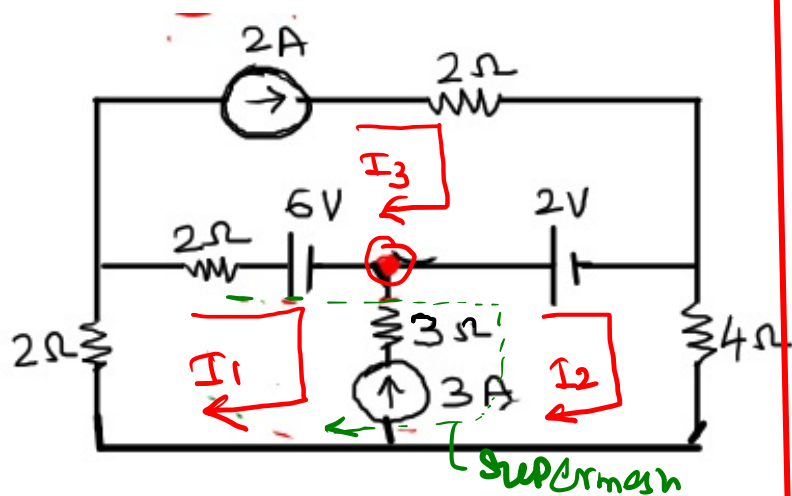

⇒ Using mesh Analysis



⇒ 2A current source on Uncommon branch of mesh-3.

$$\therefore I_3 = 2A$$

⇒ 3A Current source on Common branch of mesh ① & ② so its Supermesh.

$$I_1 + 3 = I_2$$

$$I_1 - I_2 = -3 \dots \text{①}$$

⇒ KVL to Supermesh

$$-2I_1 - 2(I_1 - I_3) - 6 - 2 - 4I_2 = 0$$

$$-2I_1 - 2I_1 + 2 \times 2 - 8 - 4I_2 = 0$$

$$-4I_1 - 4I_2 = 4$$

$$I_1 + I_2 = -1 \dots \text{②}$$


Solving ① & ②

$$I_1 = -2A, \quad I_2 = 1A$$


$$I_{4\Omega} = I_2 = 1A$$

1. Find Current Flowing in 4 Ohm Resistor using Mesh/Nodal/ Thevenin's/ Norton's /Superposition Method/ source transformation.

1A

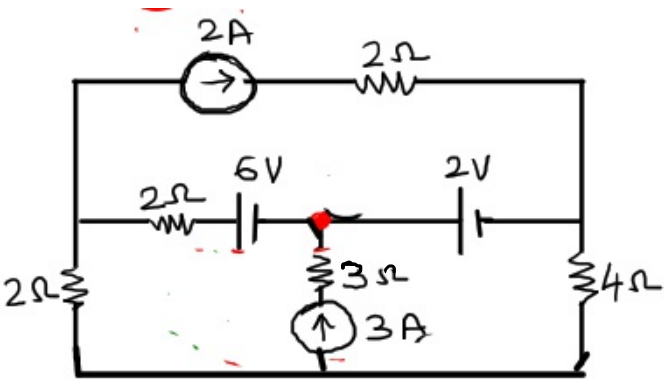

⇒ Using Nodal Analysis

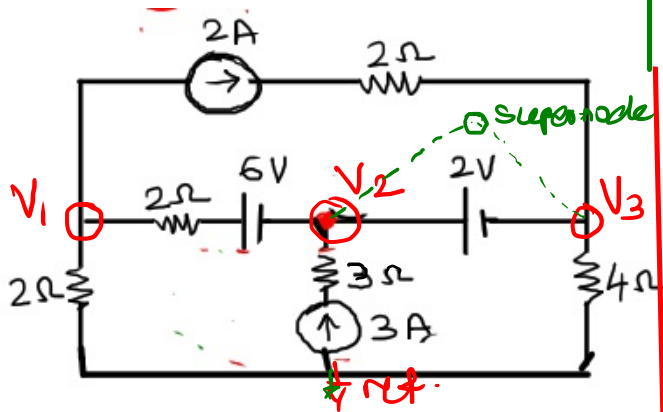

⇒ KCL at node-1.

$$\frac{V_1}{2} + \frac{V_1 - 6 - V_2}{2} + 2 = 0$$

$$V_1 + V_1 - 6 - V_2 + 4 = 0$$

$$2V_1 - V_2 = 2 \quad \text{--- (1)}$$

⇒ 2V source without series resistance with two non-ref nodes (2) (3) so supernode case.

$$V_2 - 2 - V_3 = 0$$

$$V_2 - V_3 = 2 \quad \text{--- (2)}$$

⇒ KCL at supernode.

$$-3 + \frac{V_2 + 6 - V_1}{2} + \frac{V_3}{4} - 2 = 0$$

$$\frac{2V_2 + 12 - 2V_1 + V_3}{4} = 5$$

$$-2V_1 + 2V_2 + V_3 = 8 \quad \text{--- (3)}$$


Solving (1), (2) & (3)

$$V_1 = 4V, V_2 = 6, V_3 = 4$$

$$I_{4\Omega} = \frac{V_3}{4} = \frac{4}{4} = 1A$$


1. Find Current Flowing in 4 Ohm Resistor using Mesh/Nodal/ Thevenin's/ Norton's /Superposition Method/ source transformation.

1A

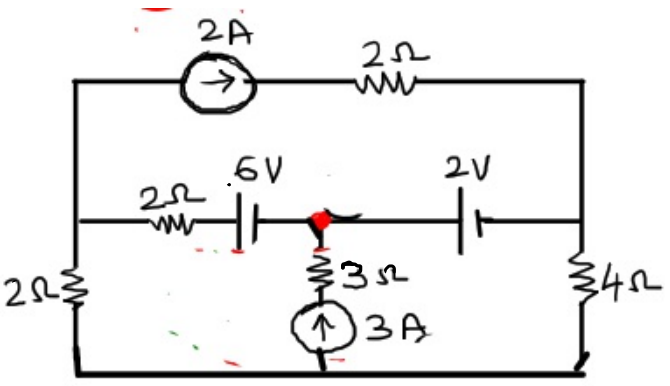

⇒ Using Thevenin's Theorem.

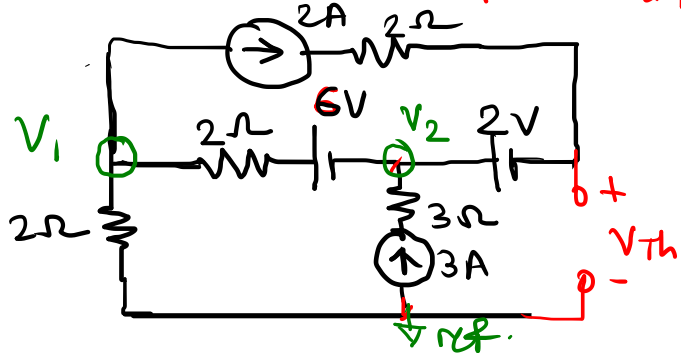→ Remove load  $R_L = 4 \Omega$  & find  $V_{th}$




⇒ Find  $V_{th}$

$$V_{th} + 2 + 6 + V_{2\Omega} + V_{2\Omega} = 0 \checkmark$$

$$V_{th} + 2 - V_2 = 0 \rightarrow$$

$$V_{th} = V_2 - 2 \Rightarrow$$

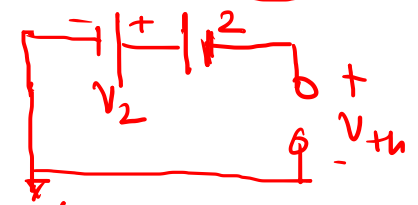

ref node

Using nodal KCL to node ①


$$\frac{V_1}{2} + \frac{V_1 - 6 - V_2}{2} + 2 = 0$$

$$V_1 + V_1 - 6 - V_2 = -4$$

$$2V_1 - V_2 = 2 \dots \textcircled{1}$$


1. Find Current Flowing in 4 Ohm Resistor using Mesh/Nodal/ Thevenin's/ Norton's /Superposition Method/ source transformation.

1A

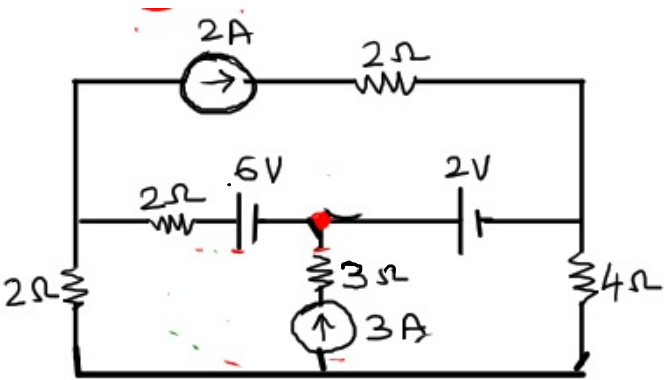

⇒ Using Thevenin's Theorem.

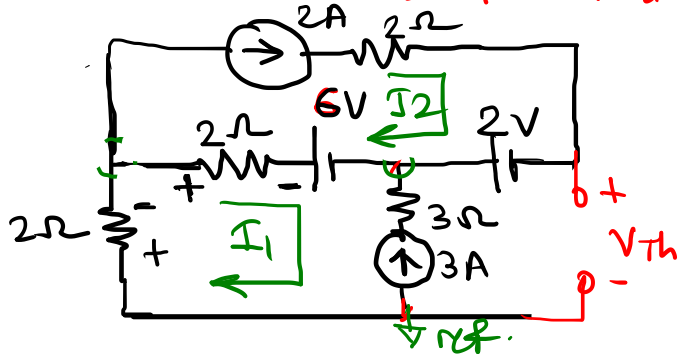→ Remove load  $R_L = 4 \Omega$  & find  $V_{th}$



⇒ Find  $V_{th}$

$$V_{th} + 2 + 6 + V_{2\Omega} + V_{2\Omega} = 0 \quad \text{--- (1)}$$

Using mesh Analysis:

KVL to mesh (I)

$$I_1 = -3A$$

$$I_2 = 2A$$

Using eqn (1)

$$V_{th} + 2 + 6 + 2(I_1 - I_2) + 2I_1 = 0$$


$$V_{th} + 2 + 6 + 2(-3 - 2) + 2 \times -3 = 0$$

$$V_{th} + 8 - 10 - 6 = 0$$

$$\boxed{V_{th} = 8V}$$


1. Find Current Flowing in 4 Ohm Resistor using Mesh/Nodal/ Thevenin's/ Norton's /Superposition Method/ source transformation.

1A

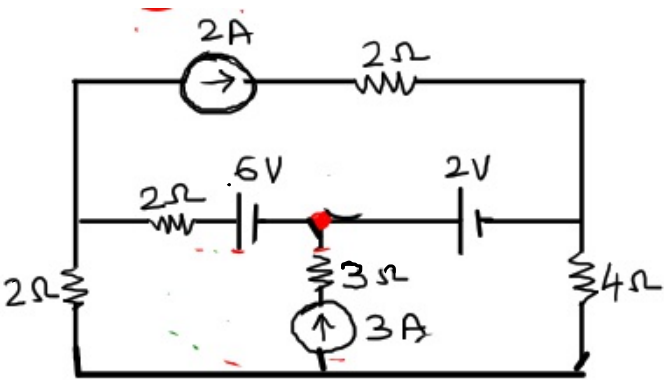

⇒ Using Thevenin's Theorem.

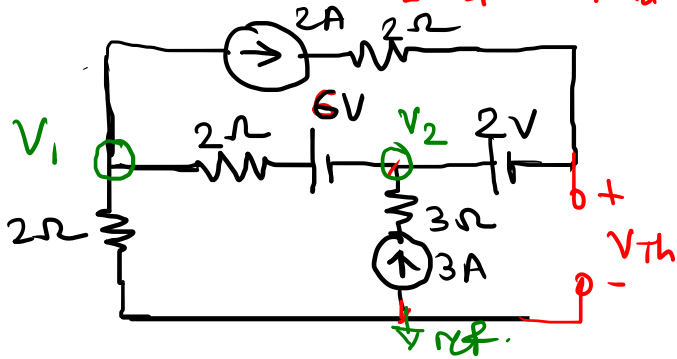→ Remove load  $R_L = 4 \Omega$  & find  $V_{th}$



KCL to node ②

$$\frac{V_2 + 6 - V_1}{2} - 3 - 2 = 0$$

$$\frac{V_2 + 6 - V_1}{2} = 5$$

$$-V_1 + V_2 = 4 \dots \textcircled{2}$$

Solving ① & ②


$$2V_1 - V_2 = 2 \dots \textcircled{1}$$

$$V_1 = 6V \quad V_2 = 10V$$


$$V_{th} = V_2 - 2 = 10 - 2 = 8V.$$

1. Find Current Flowing in 4 Ohm Resistor using Mesh/Nodal/ Thevenin's/ Norton's /Superposition Method/ source transformation.

1A

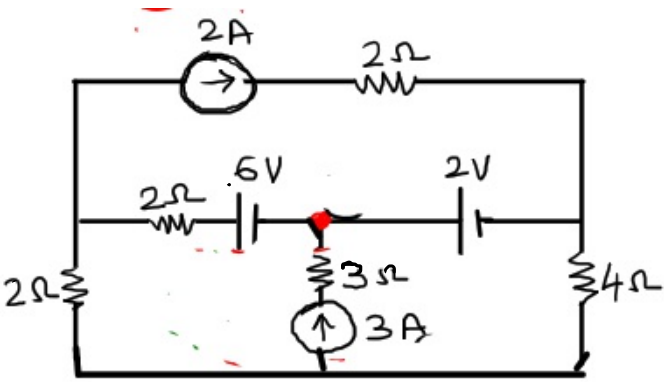


⇒ Find  $R_{th}$

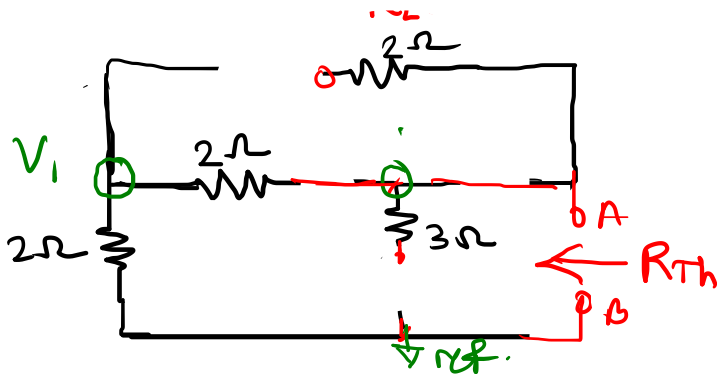

$$R_{th} = 2 + 2 = 4 \Omega$$

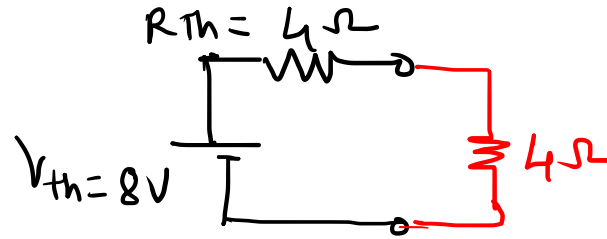⇒ Draw Thevenin's Equivalent circuit & Connect load




$$I_{4\Omega} = \frac{8}{4+4}$$

$$I_{4\Omega} = 1A$$


1. Find Current Flowing in 4 Ohm Resistor using Mesh/Nodal/ Thevenin's/ Norton's /Superposition Method/ source transformation.

1A

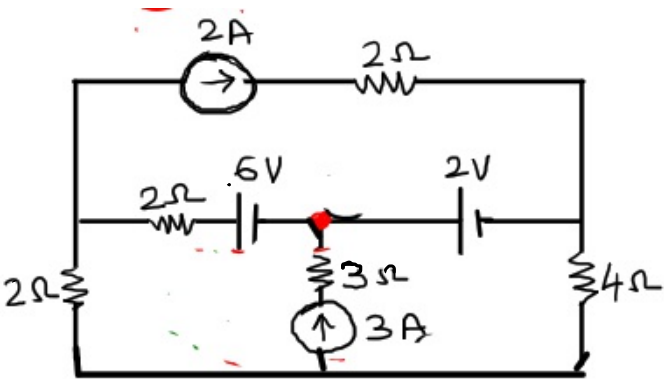

Using Norton's Theorem.

$\Rightarrow R_{th} = 4 \Omega$

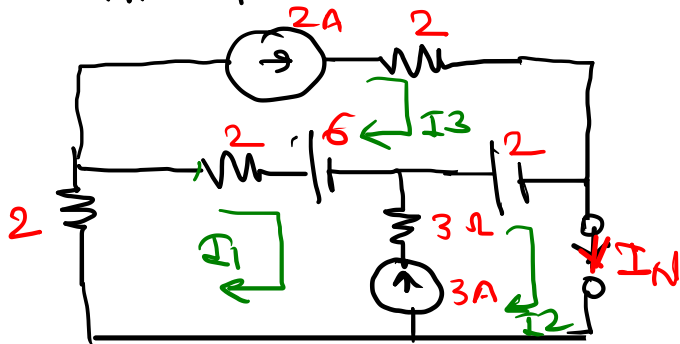

$\Rightarrow I_3 = 2A$

$\Rightarrow$  supermesh because of 3A

$I_1 - I_2 = -3 \dots \textcircled{1}$

$\Rightarrow$  KVL to supermesh.

$-2I_1 - 2(I_1 - I_3) - 6 - 2 = 0$

$-2I_1 - 2I_1 + 2I_3 - 8 = 0$

$-4I_1 + 2 \times 2 - 8 = 0$

$-4I_1 + 4 - 8 = 0$

$-4I_1 = 4 \quad \boxed{I_1 = -1A}$


using eqn ①

$I_1 - I_2 = -3 \quad \boxed{I_2 = 2A}$

$-1 - I_2 = -3$


1. Find Current Flowing in 4 Ohm Resistor using Mesh/Nodal/ Thevenin's/ Norton's /Superposition Method/ source transformation.

1A

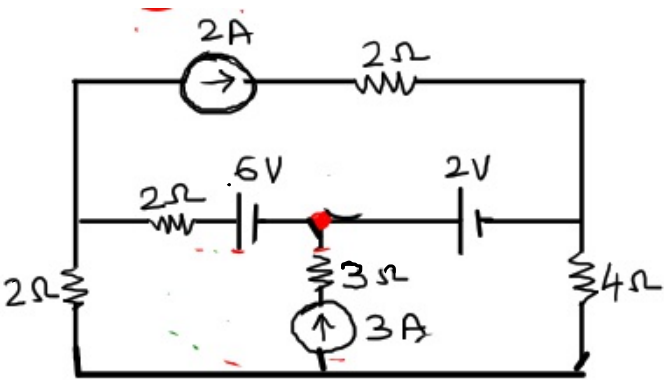


Using Norton's Theorem.

$$\Rightarrow R_{Th} = 4 \Omega$$

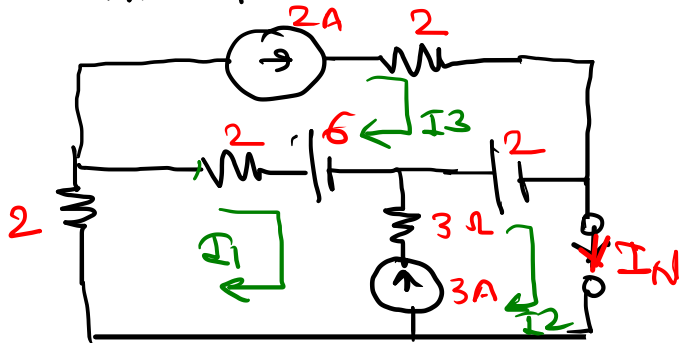

Norton's Equivalent of  
Connect load.

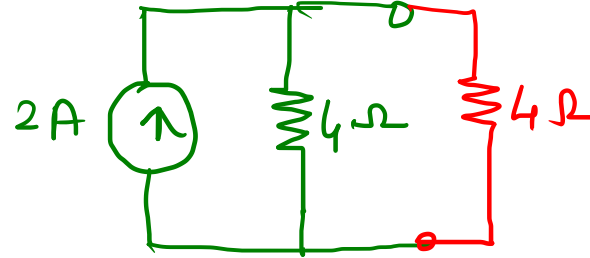


$$I_{4\Omega} = \frac{4 \times 2}{4 + 4}$$

$$I_{4\Omega} = 1 \text{ A}$$




2. Find Current in 15 Ohm Resistor

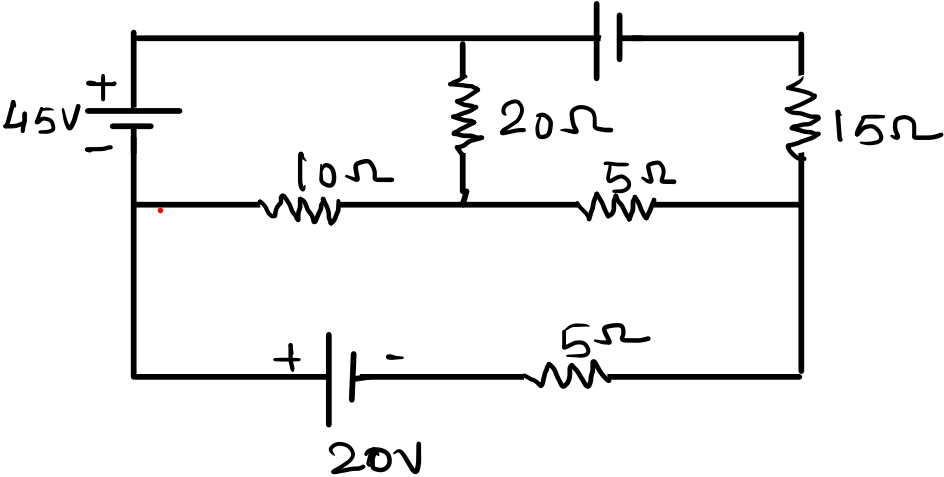


(3.54A)

### 3. Find Current in 5 Ohm Resistor

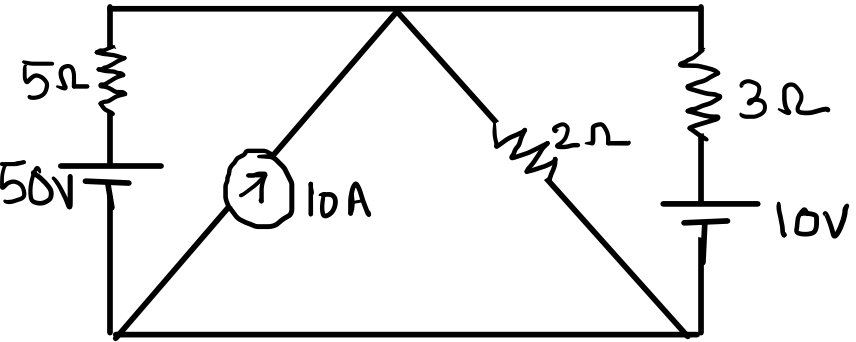

5.485  
↑

#### 4. Find Current in 4 Ohm Resistor

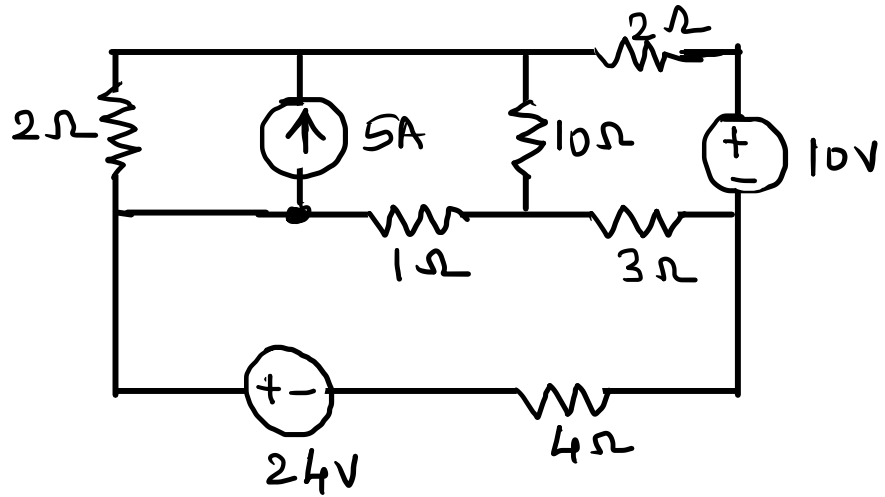

4.1 ←